

63. || What is the current through the $10\ \Omega$ resistor in **FIGURE P31.63**?

Is the current from left to right or right to left?

$$R_{10} = 10\ \Omega$$

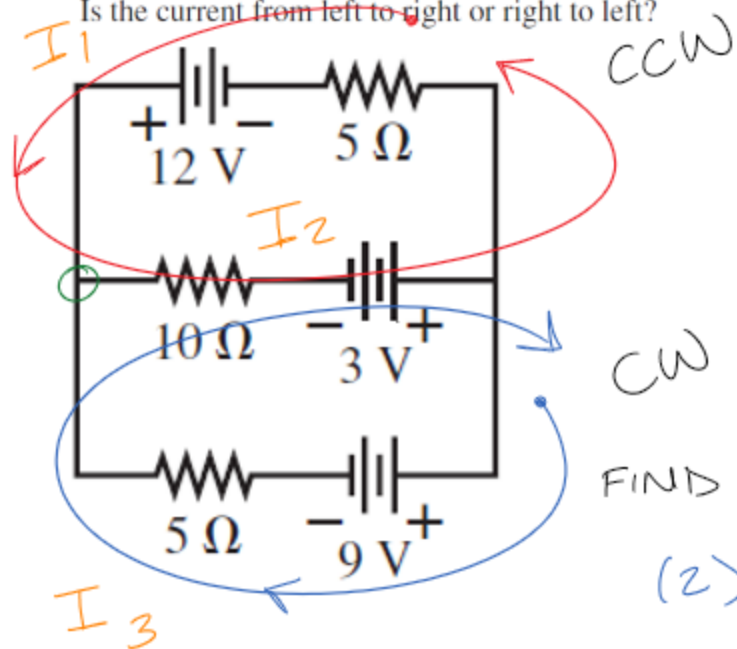


FIGURE P31.63

$$(1) \sum V = 0 \rightarrow +12 - I_2 R_{10} + 3 - I_1 R_5 = 0$$

$$(2) \sum V = 0 \rightarrow +3 - 9 - I_3 R_5 - I_2 R_{10} = 0$$

$$(3) I_{IN} = I_{OUT} \rightarrow I_1 + I_3 = I_2$$

FIND I_2

$$(2) \rightarrow I_3 = \frac{-6 - I_2 R_{10}}{R_5}$$

$$(1) \rightarrow I_1 = \frac{15 - I_2 R_{10}}{R_5}$$


$$(3) \rightarrow I_2 = \frac{15 - I_2 R_{10}}{R_5} + \frac{-6 - I_2 R_{10}}{R_5}$$

$$I_2 R_5 = 9 - 2I_2 R_{10}$$

$$I_2 [R_5 + 2R_{10}] = 9 \rightarrow I_2 = \frac{9}{5 + 2(10)} = \boxed{0.36\text{ A}}$$

12. | The loop in FIGURE EX33.12 is being pushed into the 0.20 T magnetic field at 50 m/s. The resistance of the loop is 0.10 Ω . What are the direction and the magnitude of the current in the loop?

FIGURE EX33.12

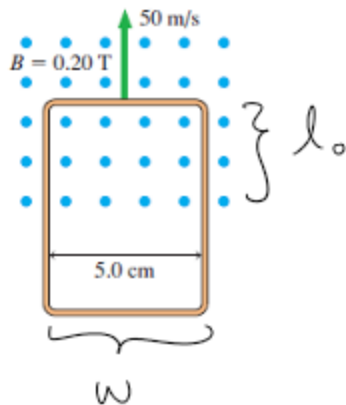

FIND I

$$\Phi = \oint \vec{B} \cdot d\vec{A} \rightarrow BA = B(lw)$$

$$\mathcal{E} = -\frac{d\Phi}{dt} = -\frac{d}{dt}[B lw]$$

$$= -Bw \frac{d}{dt}[l]$$

$$= -Bwv$$

$$V = IR \rightarrow I = \frac{V}{R} = \frac{|\mathcal{E}|}{R} = \frac{Bwv}{R}$$

$$= \frac{(0.20 \text{ T})(0.05 \text{ m})(50 \text{ m/s})}{(0.10 \Omega)} = \boxed{5 \text{ A}}$$