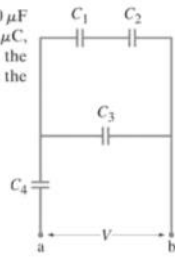


30. (II) Suppose in Fig. 24-23 that  $C_1 = C_2 = C_3 = 16.0 \mu\text{F}$  and  $C_4 = 28.5 \mu\text{F}$ . If the charge on  $C_2$  is  $Q_2 = 12.4 \mu\text{C}$ , determine the charge on each of the other capacitors, the voltage across each capacitor, and the voltage  $V_{ab}$  across the entire combination.



DISCLAIMER: THIS IS CH 24, 25 WHICH IS BEFORE KIRCHHOFF'S LAW STUFF

FIND  $Q_1, Q_3, Q_4$  &  $V_1, V_2, V_3, V_4$

$$C_{12} = \left[ \frac{1}{C_1} + \frac{1}{C_2} \right]^{-1} = \left[ \frac{1}{16} + \frac{1}{16} \right]^{-1} = \left[ \frac{2}{16} \right]^{-1} = 8 \mu\text{F}$$

$$C_{123} = C_{12} + C_3 = 8 + 16 = 24 \mu\text{F}$$

$$C_{1234} = \left[ \frac{1}{C_{123}} + \frac{1}{C_4} \right]^{-1} = \left[ \frac{1}{24} + \frac{1}{28.5} \right]^{-1} \approx 13 \mu\text{F}$$

$$\text{SINCE } Q_2 = 12.4 \mu\text{C}, \quad V_2 = \frac{Q_2}{C_2} = \frac{12.4}{16} = \boxed{0.775 \text{ V}}$$

KEEP IN MIND:

↳ DEVICES IN PARALLEL ~ SAME  $V$





↳ DEVICES IN SERIES ~ SAME  $Q$

SINCE  $Q_1$  &  $Q_2$  IN SERIES:  $Q_1 = Q_2$

$$\rightarrow Q_1 = Q_2$$

$$= C_2 V_2 = (16)(0.775) = \boxed{12.4 \mu\text{C}}$$
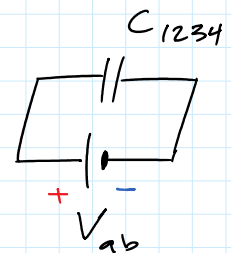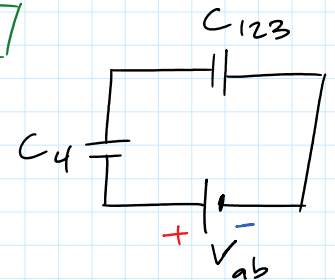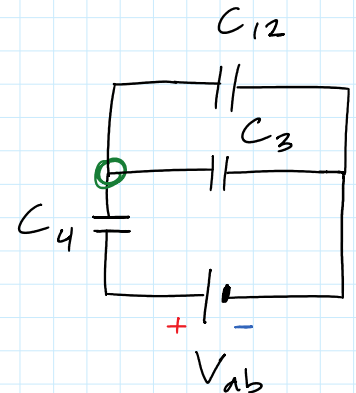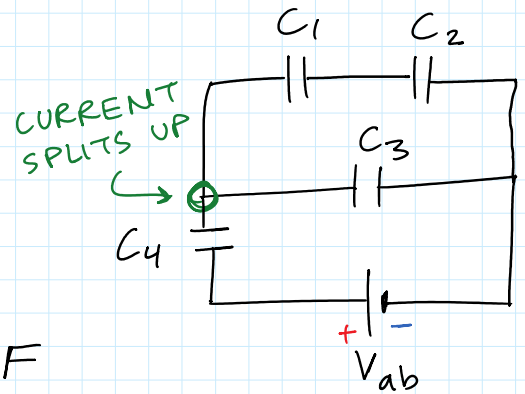
$$\rightarrow V_2 = \frac{Q_2}{C_2} = \frac{12.4}{16} = \boxed{0.775 \text{ V}} \sim V_1 = V_2 \text{ SINCE } C_1 = C_2$$



ALSO: VOLTAGES IN SERIES ARE ADDED, SO  $V_{12} = V_1 + V_2 = 2(0.775)$

$$= 1.55 \text{ V}$$

SINCE  $C_{12}$  &  $C_3$  IN PARALLEL,  $V_{12} = V_3$

$$\rightarrow V_3 = V_2 = \boxed{1.55 \text{ V}}$$

IT TURNS OUT  $V_{123} = V_{12} = V_3$  SINCE THESE ARE ALL PARALLEL

SINCE  $C_{123}$  &  $C_4$  IN SERIES,  $Q_{123} = Q_4 = Q_{1234} = Q_{\text{TOTAL}}$

$$\rightarrow Q_4 = Q_{123}$$

$$= C_{123} V_{123} = (24)(1.55) = \boxed{37.2 \mu\text{C}}$$

$$\rightarrow V_4 = \frac{Q_4}{C_4} = \frac{37.2}{28.5} = \boxed{1.305 \text{ V}}$$

$$\text{SINCE } V_{123} \text{ \& } V_4 \text{ IN SERIES, } V_{1234} = V_{123} + V_4 = 1.55 + 1.305 = \boxed{2.855 \text{ V}}$$

GOING FROM + TO - ON THE BATTERY, THE VOLTAGE

GOES FROM  $V_{ab}$  TO ZERO SO  $V_{ab} = V_4 + V_{123} = V_{1234}$

$$= \boxed{2.855 \text{ V}}$$

30.  $C_1$  and  $C_2$  are in series, so they both have the same charge. We then use that charge to find the voltage across each of  $C_1$  and  $C_2$ . Then their combined voltage is the voltage across  $C_3$ . The voltage across  $C_3$  is used to find the charge on  $C_3$ .

$$Q_1 = Q_2 = 12.4 \mu\text{C}; V_1 = \frac{Q_1}{C_1} = \frac{12.4 \mu\text{C}}{16.0 \mu\text{F}} = 0.775 \text{ V}; V_2 = \frac{Q_2}{C_2} = \frac{12.4 \mu\text{C}}{16.0 \mu\text{F}} = 0.775 \text{ V}$$

$$V_3 = V_1 + V_2 = 1.55 \text{ V}; Q_3 = C_3 V_3 = (16.0 \mu\text{F})(1.55 \text{ V}) = 24.8 \mu\text{C}$$

From the diagram,  $C_4$  must have the same charge as the sum of the charges on  $C_1$  and  $C_3$ . Then the voltage across the entire combination is the sum of the voltages across  $C_4$  and  $C_3$ .


$$Q_4 = Q_1 + Q_3 = 12.4 \mu\text{C} + 24.8 \mu\text{C} = 37.2 \mu\text{C}; V_4 = \frac{Q_4}{C_4} = \frac{37.2 \mu\text{C}}{28.5 \mu\text{F}} = 1.31 \text{ V}$$

$$V_{ab} = V_4 + V_3 = 1.31 \text{ V} + 1.55 \text{ V} = 2.86 \text{ V}$$

Here is a summary of all results.

$$\boxed{Q_1 = Q_2 = 12.4 \mu\text{C}; Q_3 = 24.8 \mu\text{C}; Q_4 = 37.2 \mu\text{C}} \\ \boxed{V_1 = V_2 = 0.775 \text{ V}; V_3 = 1.55 \text{ V}; V_4 = 1.31 \text{ V}; V_{ab} = 2.86 \text{ V}}$$

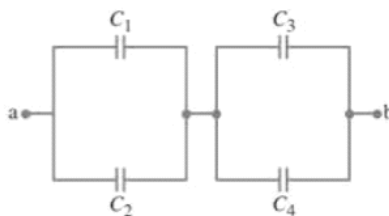33. (II) Suppose in Problem 32, Fig. 24-25, that  $C_1 = C_3 = 8.0 \mu\text{F}$ ,  $C_2 = C_4 = 16 \mu\text{F}$ , and  $Q_3 = 23 \mu\text{C}$ . Determine (a) the charge on each of the other capacitors, (b) the voltage across each capacitor, and (c) the voltage  $V_{ba}$  across the combination.



33. (a) The voltage across  $C_3$  and  $C_4$  must be the same, since they are in parallel.

$$V_3 = V_4 \rightarrow \frac{Q_3}{C_3} = \frac{Q_4}{C_4} \rightarrow Q_4 = Q_3 \frac{C_4}{C_3} = (23 \mu\text{C}) \frac{16 \mu\text{F}}{8 \mu\text{F}} = \boxed{46 \mu\text{C}}$$

The parallel combination of  $C_3$  and  $C_4$  is in series with the parallel combination of  $C_1$  and  $C_2$ , and so  $Q_3 + Q_4 = Q_1 + Q_2$ . That total charge then divides between  $C_1$  and  $C_2$  in such a way that

$$V_1 = V_2.$$

$$Q_1 + Q_2 = Q_3 + Q_4 = 69 \mu\text{C} ; V_1 = V_2 \rightarrow \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{69 \mu\text{C} - Q_1}{C_2} \rightarrow$$

$$Q_1 = \frac{C_1}{C_2 + C_1} (69 \mu\text{C}) = \frac{8.0 \mu\text{F}}{24.0 \mu\text{F}} (69 \mu\text{C}) = \boxed{23 \mu\text{C}} ; Q_2 = 69 \mu\text{C} - 23 \mu\text{C} = \boxed{46 \mu\text{C}}$$

Notice the symmetry in the capacitances and the charges.

- (b) Use Eq. 24-1.

$$V_1 = \frac{Q_1}{C_1} = \frac{23 \mu\text{C}}{8.0 \mu\text{F}} = 2.875 \text{ V} \approx \boxed{2.9 \text{ V}} ; V_2 = V_1 = \boxed{2.9 \text{ V}}$$

$$V_3 = \frac{Q_3}{C_3} = \frac{23 \mu\text{C}}{8.0 \mu\text{F}} = 2.875 \text{ V} \approx \boxed{2.9 \text{ V}} ; V_4 = V_3 = \boxed{2.9 \text{ V}}$$

- (c)  $V_{ba} = V_1 + V_3 = 2.875 \text{ V} + 2.875 \text{ V} = 5.75 \text{ V} \approx \boxed{5.8 \text{ V}}$